

Annexure No.:

## EXPERIMENT-04

Aim : To verify ideal value and practical value of voltage regulator ICs.

Apparatus : Connecting wires, trainer kit, multimeter.

Theory : A power supply is an electronic device that supplies electric energy to an electrical load.

- Type →
- ① DC power supply
  - ② AC power supply
  - ③ switched mode power supply.
  - ④ uninterruptible power supply.

DC power supply :

① Linear regulator.


converts varying voltage to constant DC voltage and reduce ripple / noise.

② Regulated AC to DC power supply converts AC into constant DC using a rectification and gives stable output.

construction and working regulated DC power supply.



## Diagram:

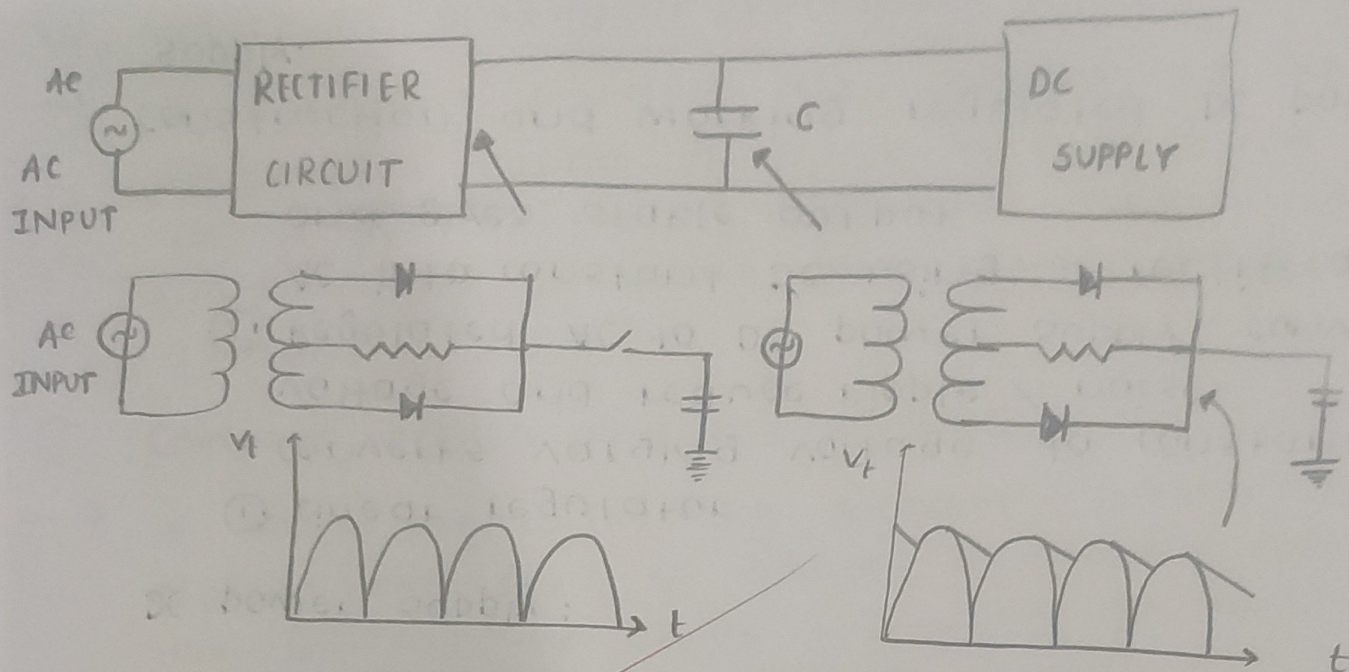

Observation Table:

| IC   | Ideal value | Practical value |
|------|-------------|-----------------|
| 7805 | +5V         | +5.05           |
| 7905 | -5V         | -5.05           |
| 7812 | +12V        | +12.05          |
| 7912 | -12V        | -12.05          |



Annexure No.:

from the 7095 IC Regulator 1<sup>st</sup> pin is ground and pin is input 3rd pin is output to measure the output voltage and 1 are connected as positive and negative pins.

### Conclusion:

- ① from the above experiment we were able to the working of DC regulator power supply.

*Abey*  
28/12

oltage

the  
accept